

ECEN 214 Lab 3

Equivalent Networks and Superposition

Team: Josh Ortiz, James Robinson

Section 502

TA: Yichi Zhang

Date Performed: 2/19/18

Date Lab Report Due: 2/26/18

Task 1

Procedure

1. Construct the circuit below

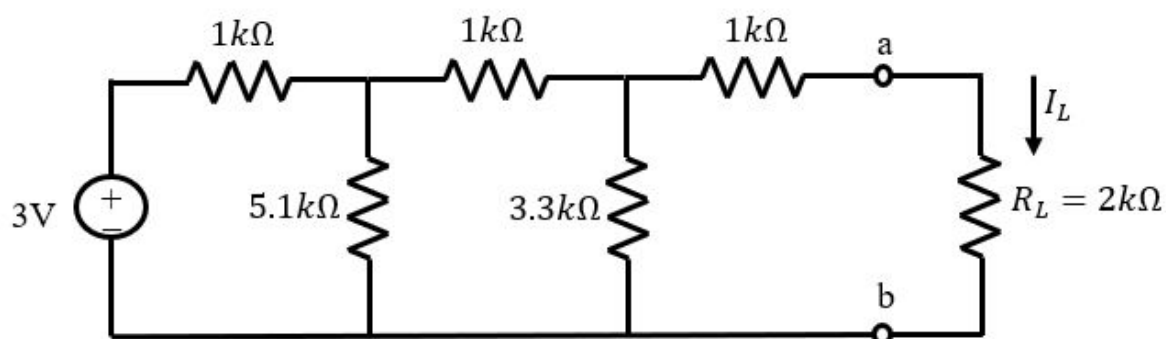


Figure 3.4

2. Measure the voltage across the resistor R_L for 2 values of R_L not equal to $2k\Omega$
3. Measure the voltage across the resistor R_L for R_L equal to $2k\Omega$
4. Calculate the Thevenin equivalent of the circuit

Data Tables

$R_L (\Omega)$	$V_L (V)$
100	.1304
3300	1.799
2000	1.4286

Sample Calculations

$$V_L / R_L = I_L$$

$$3 = I_L * (R_L + R_{th})$$

1.

$$.1304 / 100 = I_L = .001304$$

$$3 = .001304 * (100 + R_{th})$$

$$R_{th} = 2200$$

2.

$$1.799 / 3300 = I_L = .000552$$

$$3 = .000545 * (3300 + R_{th})$$

$$R_{th} = 2200$$

$$R_{th} = 2200$$

Discussion

I arrived at my Thevenin equivalent for the circuit pictured above by taking the voltage measurements, V_L , for different values of the load resistor, R_L . I could then set up a system of equations to determine what the total resistance of the rest of the circuit was (all those resistors other than R_L). This allowed me to arrive at an accurate value of R_{th} and set up a Thevenin model of the circuit to arrive at the correct values for V_L .

Task 2 & 3

Task 2 Procedure

1. Construct the circuit below

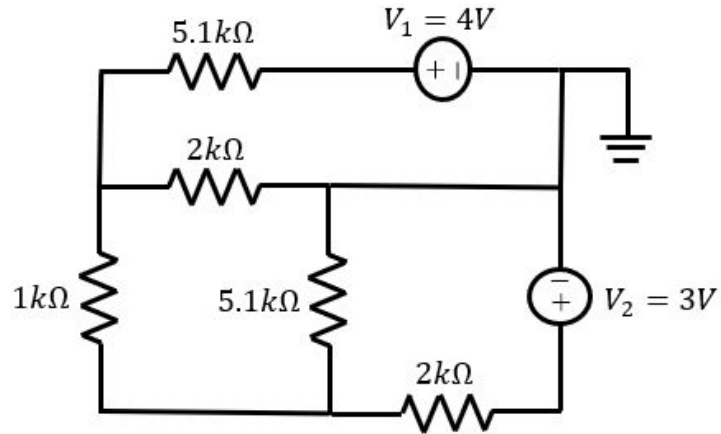


Figure 3.5

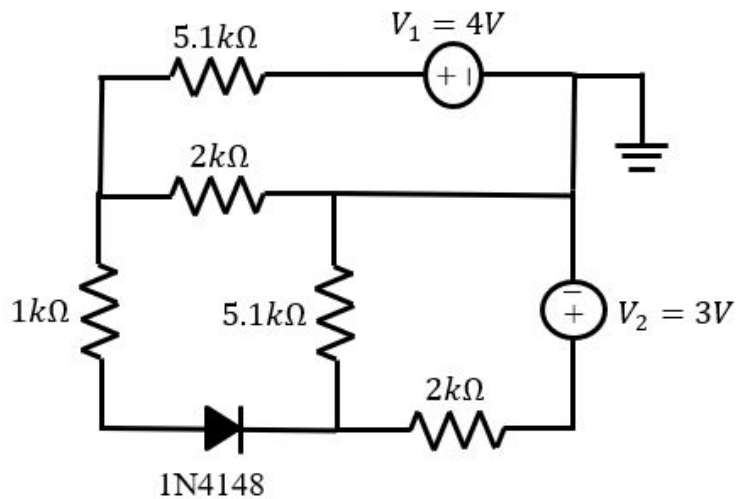


Figure 3.6

2. Measure and record the voltage across the 1k resistor.
3. To test the principle of superposition, measure the voltage across the 1k resistor when only the 4V battery is connected, and also when only the 3V battery is connected.

Task 3 Procedure

4. Repeat steps 2 and 3 of the task 2 procedure except insert a diode so the circuit so it looks like the one below.

Data Tables

Task 2 Table

Parameter	Measured (mA)	Calculated (mA)	% difference	SPICE (mA)	% difference (SPICE to measured)
VL	.523	-.265	-151%	-.265	-151%
VL,1	.739	.296	-60%	.291	-61%
VL,2	-.216	-.558	-158%	-.556	-157%
VL,1+VL,2	.523	-.265	-151%	-.265	-151%

Task 3 Table

Parameter	Measured (mA)	Calculated (mA)	% difference	SPICE (mA)	% difference (SPICE to measured)
VL	0	0	0%	0	0%
VL,1	.152	.161	5.9%	.161	5.9%
VL,2	0	0	0%	0	0%
VL,1+VL,2	.152	.161	5.9%	.161	5.9%

Sample Calculations



Task 2

$$5.1k \parallel 2k = 1436.6$$

Voltage divider


$$3 \cdot \frac{2.4}{(2+2.4)} = 1.36$$

$$I_2 = \frac{-1.36}{2436.6} = -.558mV$$

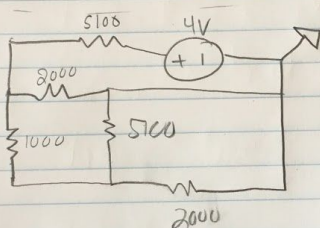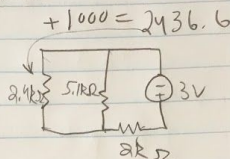

$$5100 \parallel 2000 = 1436.6$$


$$2000 \parallel 2436.6 = 1098$$

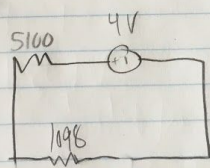

Voltage divider

$$V = \frac{1098}{1098 + 2436.6} \cdot 4 = 1.720V$$

$$I = 1.720 / 2436.6 = .296mA$$

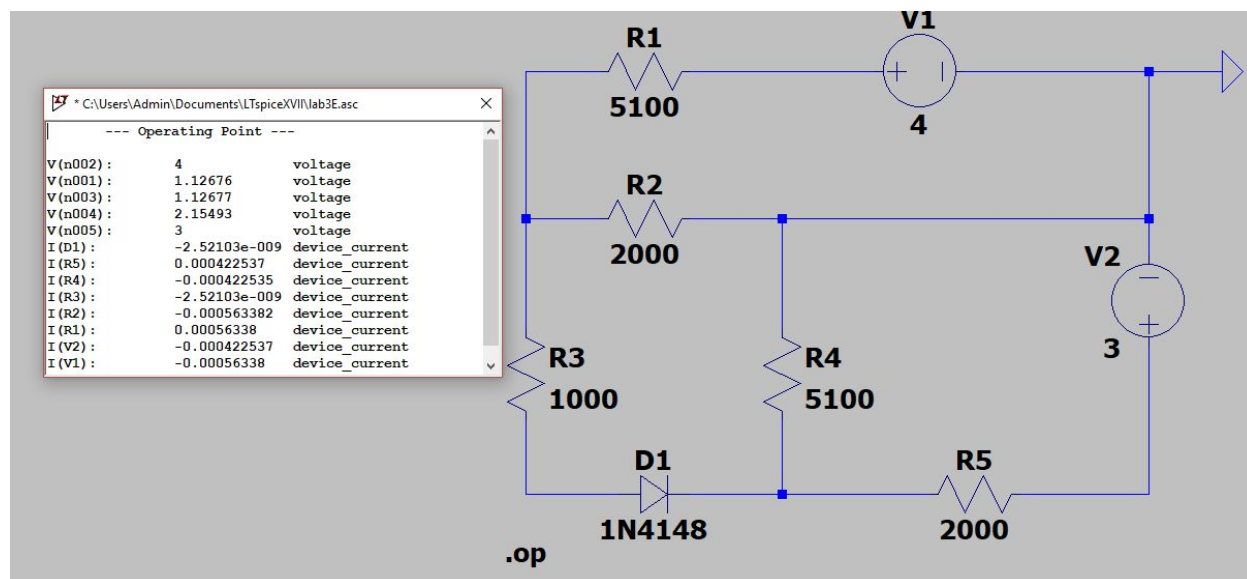

Discussion

Superposition worked to figure out the current across the 1k resistor in task 2 but not in task 3. This is because the diode is a non linear element; it will only allow current to flow in one direction. That means when the 3 V battery was the current flowing through the 1k resistor was zero. The only time that current could flow through is when just the 4 V battery was connected. Resistors are linear elements because they obey Ohm's law, a diode does not. That is what makes a circuit element linear, its current, voltage, and resistance being related in a linear way.