

Lab 6: Non-Ideal Sources

Team: Joshua Ortiz, James Robinson

ECEN 214-502

TA: Yichi Zhang

Date Performed: 03/26/19

Date Report Due: 04/02/19

Procedure

Task 1:

1. Create the circuit below with the resistor and capacitor values chosen from the prelab.

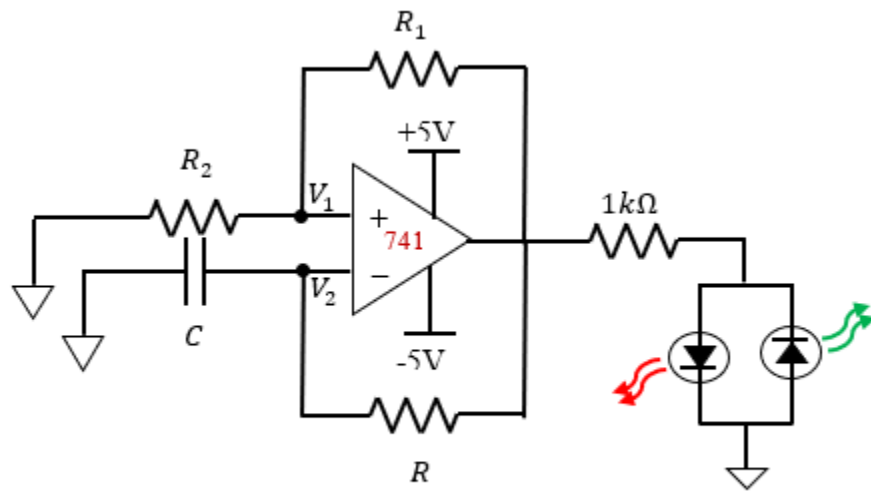


Figure 6.5 – A Flashing LED Circuit

2. Make sure the LEDs are switching off by flashing on and off by one second. If not, the component values are not correct and must be recalculated.
3. Use your oscilloscope on your AD2 to display both $V_1(t)$ and $V_2(t)$.
4. Adjust your vertical scale so that the waveforms occupy about 70% scale so that approximately two periods of the waveforms are shown.
5. Take a screenshot of the waveform.
6. Use the scope to measure
 - a. Actual frequency of oscillation.
 - b. Peak-to-peak voltage.
 - c. Root-Mean-Square (RMS) Voltage.

Task 2:

1. Replace the two resistors R_1 and R_2 with a $10k\Omega$ potentiometer. The circuit should look the one below (a diagram of the potentiometer is also given).


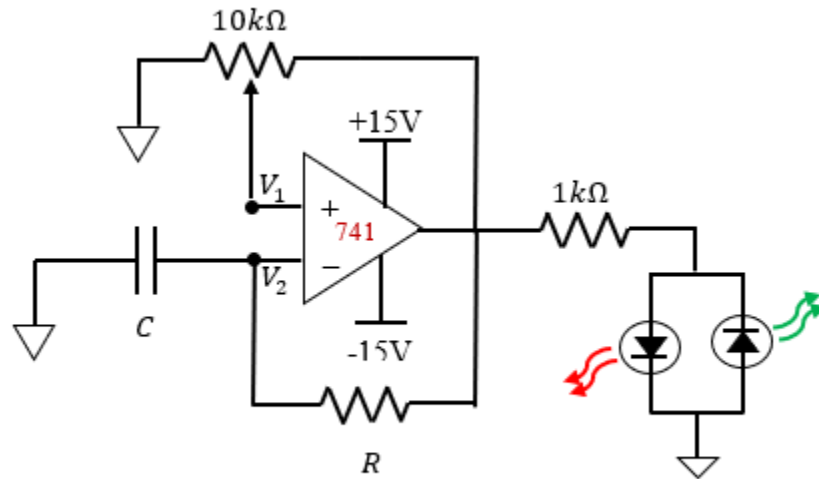
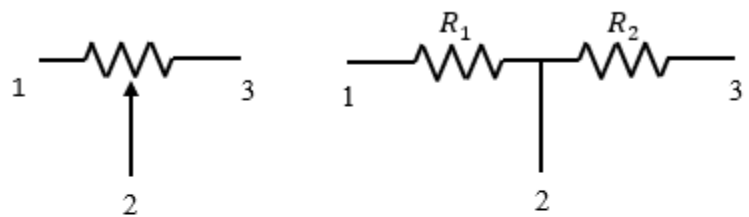


Figure 6.7 – Modified Flashing LED Circuit for Task 2.

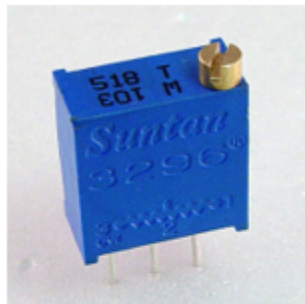

(a)

(b)

(c)

Figure 6.6 – (a) A typical potentiometer, (b) its schematic, and (c) an equivalent circuit.

2. Use your oscilloscope on your AD2 to display both $V_1(t)$ and $V_2(t)$.
3. Adjust the potentiometer until the circuit oscillates at a frequency of 2Hz.
4. Take a screenshot of the waveform.
5. Shut the circuit off and measure the corresponding R_1 and R_2 values of the potentiometer.

6. Record this data and calculate the voltage division ratio, γ .
7. Replace resistor R with one at half its value.
8. Measure and record the new frequency of oscillation.
9. Take a screenshot of the waveform.
10. Last repeat steps 3-6 with the new resistor value.

Data Tables

Task 1: Circuit Component and Measured Values

R_1	$2.5k\Omega$
R_2	$2.5k\Omega$
C	$10\mu F$
R	$100k\Omega$
$Peak2Peak$	$1.79V$
f	$1.026Hz$
$V_1 RMS$	$888 mV$
$V_2 RMS$	$520 mV$

Task 2A: Potentiometer Measurements

R_1	8.37Ω
R_2	$1.4k\Omega$
C	$10\mu F$
R	$100k\Omega$
$Peak2Peak$	$1.04V$
f	$1.95Hz$
$V_1 RMS$	$521 mV$
$V_2 RMS$	$304 mV$
$\gamma = \frac{R_2}{R_1 + R_2}$	0.143

Task 2B: Potentiometer Measurements

R_1	8.37 Ω
R_2	1.4k Ω
C	10 μF
R	100k Ω
<i>Peak2Peak</i>	1.06V
f	3.8Hz
$V_1 RMS$	527 mV
$V_2 RMS$	309 mV
$\gamma = \frac{R_2}{R_1 + R_2}$	0.143

Task 2C: Potentiometer Measurements

R_1	7.31 Ω
R_2	2.37 Ω
C	10 μF
R	50k Ω
<i>Peak2Peak</i>	1.86V
f	2.05Hz
$V_1 RMS$	930 mV
$V_2 RMS$	543 mV
$\gamma = \frac{R_2}{R_1 + R_2}$	0.244


Sample Calculations:

$$\gamma = \frac{R_2}{R_1 + R_2}$$


$$\%Error_1 = \left| \frac{Actual - Experimental}{Actual} \right| \times 100$$

Screenshot


Task 1:

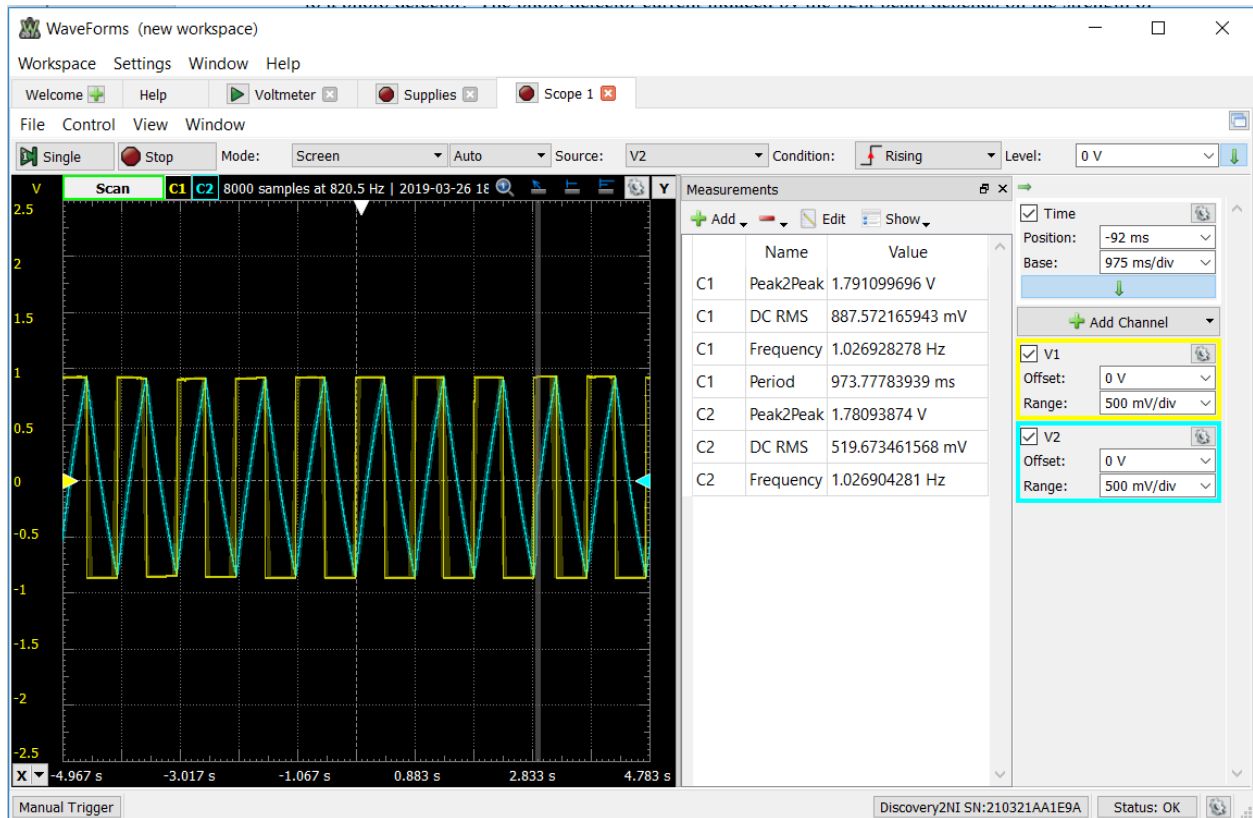

Task2A:

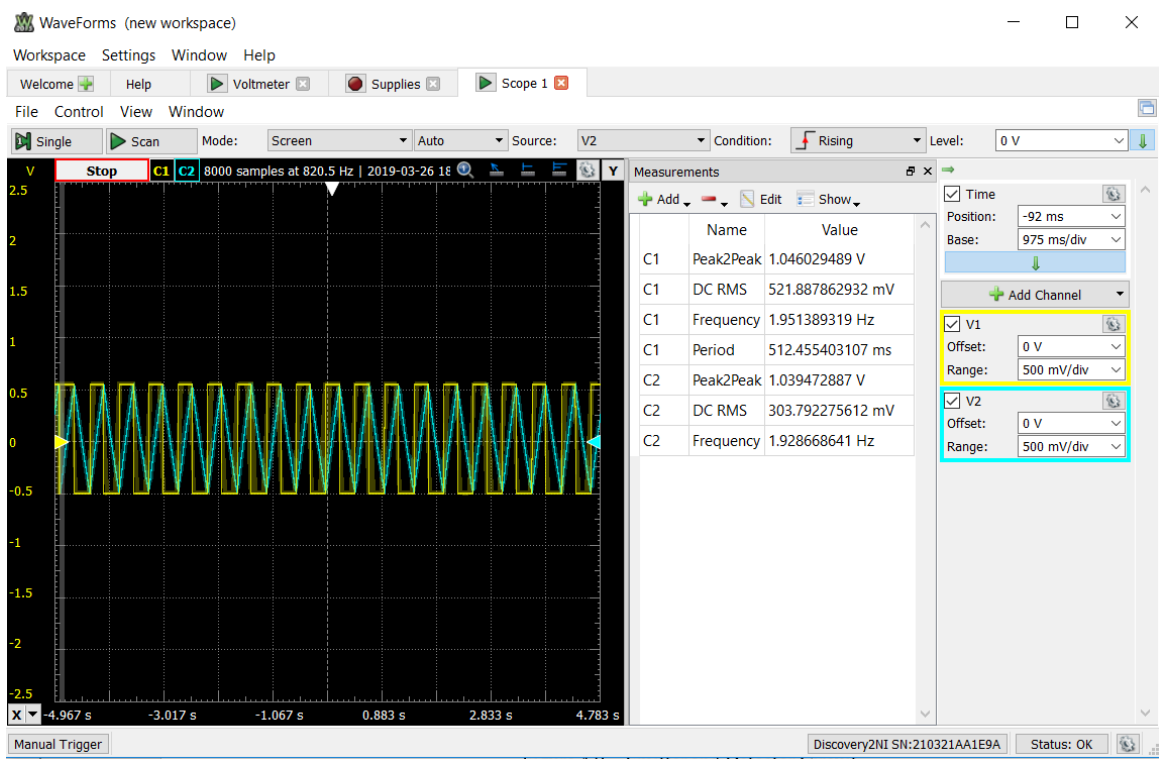

Task2B:

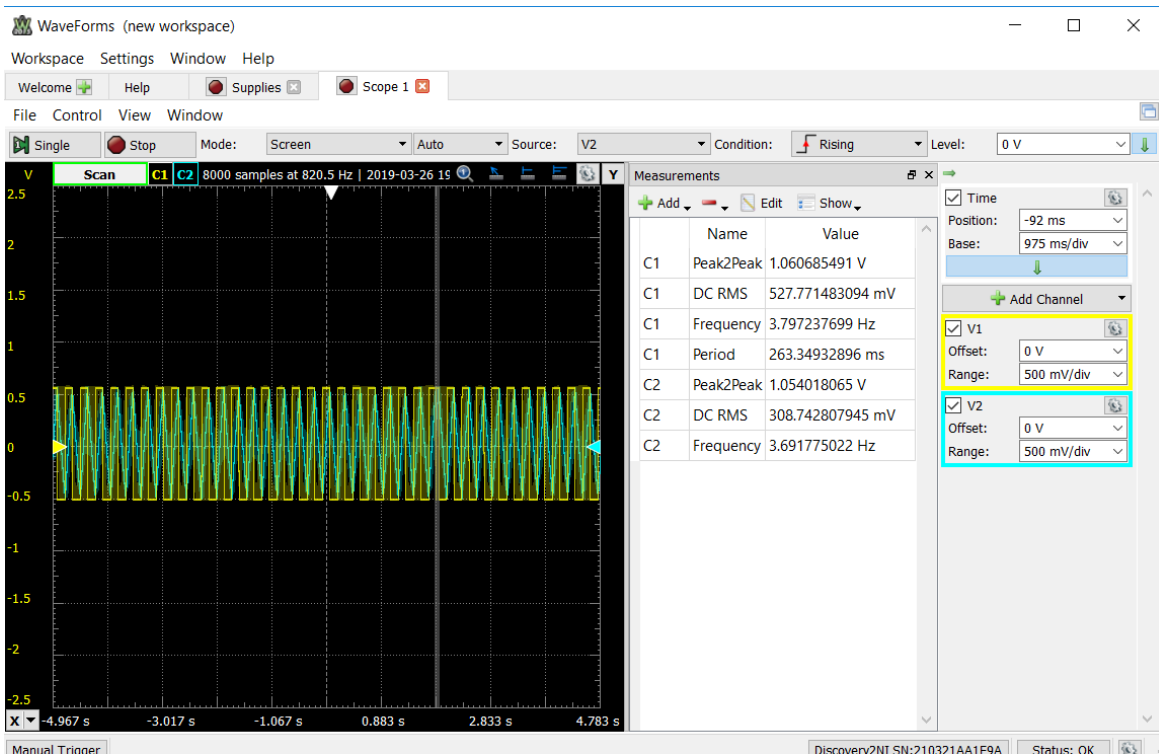

Task2C:

